

CSC9R6 Computer Design



Practical Digital Logic

References



■ (for this part of CSC9R6)

- Hamacher et al: Computer Organization App A.

■ In library

- Floyd: Digital Fundamentals Ch 1, 3-6, 8-10

- web page: www.prenhall.com/floyd/

- Mano: Computer System Architecture Ch 1 and 2

- Green: Digital Electronics Ch 1, 3 - 11

■ Tools

- Digital Works

- Electronics Workbench

What's it all about?



- Computers manipulate information
 - (already seen - Brookshear machine, programming languages, application programs)
- This part of the course looks at the hardware operations of a computer system
 - can mean CPU, I/O, RAM, devices ... anything with a circuit or chip
- Specifically, we look at
 - computer organisation
 - the way basic hardware components work
 - the way they are connected together


Binary Information



- How is data represented inside a digital computer?
 - Using groups of digits (bits) in the binary number system (0 to 1 - very reliable)
- At an even lower level, binary information is physically represented
 - By electrical signals (logic levels HIGH and LOW) e.g. in TTL 2 - 5 volts = 1 and 0 - 0.8 volts = 0
- The digital circuits accept signals of this type and produce signals of this type.

Waveforms

 
- Voltage levels constantly change back and forth from 0 to 1 during processing. This gives a **digital waveform**.
- A **Positive** Pulse is when a logic level switches from 0 to 1 and back to 0. (So a Negative pulse is ...?)




- Ideal pulses - change happens instantaneously.

Periodic Pulses

 - Often in a digital system the waveform is a series of pulses.
- E.g. the clock




- A waveform carries information

 

- For example, 1010011010

Timing Diagrams

 - A timing diagram is a graph of digital waveforms showing the relationship between the waveforms.



Gates (Logic Operations)



- Binary information is manipulated and processed through **gates**
 - Gates are the hardware embodiment of particular functions - for a given gate certain patterns of input signals produce certain patterns of output.

Gates



- Gates have several representations:
 - A graphic symbol (syntax really)
 - A name (more syntax)
 - A function (semantics)
 - Boolean algebra (familiar from 3111)
 - Algebraic expression (uses literals and logic ops)
 - A truth table (shows all possible inputs and output)
- We're going to see all of them! Each is important for different tasks.

AND


■ Algebraically

$$x = A.B$$

or

$$x = AB$$

■ Pictorially

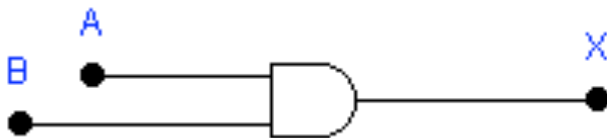


■ Truth Table

A	B	x
0	0	0
0	1	0
1	0	0
1	1	1

- i.e. true if both inputs are true
- You can think of 1 (HIGH) as TRUE and 0 (LOW) as FALSE (because AND is just the familiar Boolean AND)

AND (there's more)

 - AND can also be extended to more inputs
- $x = A.B.C$



■ Truth Table

A	B	C	x
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

- Only outputs a 1 if all inputs are 1

OR

■ $x = A + B$




■ Truth table

A	B	x
0	0	0
0	1	1
1	0	1
1	1	1

NOT

■ $x = A'$

■ also written $x = \overline{A}$

 

■ Truth table

A	x
0	1
1	0

NAND (Not AND)

■ $x = (A.B)'$




■ Truth Table

A	B	x	[AND was]
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

■ NAND is a *universal* gate

NOR (Not OR)

■ $x = (A + B)'$

 


■ Truth table

A	B	x	[OR was]
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

■ NOR is a *universal* gate

XOR (Exclusive OR)

■ $x = (A + B).(A.B)'$
 $= A.B' + A'.B$

 

■ Truth Table

A	B	x
0	0	0
0	1	1
1	0	1
1	1	0

■ either A or B but not both.


Putting it Together



- Using different notations also allows us to design in a convenient way (algebra) and translate to hardware, or to take a circuit and determine its function.

Example 1

- Start with a circuit

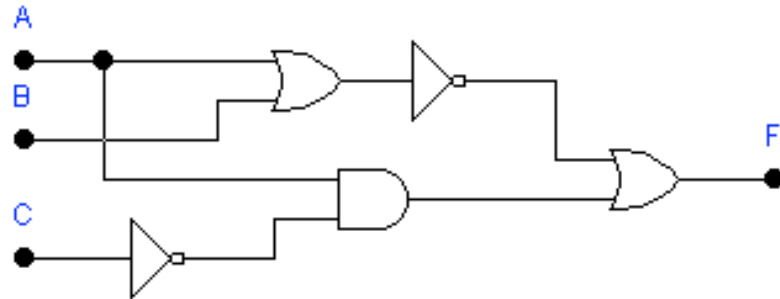


$$F = (A+B)' + (A.C')$$

A	B	C	$(A+B)'$	$A.C'$	F
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

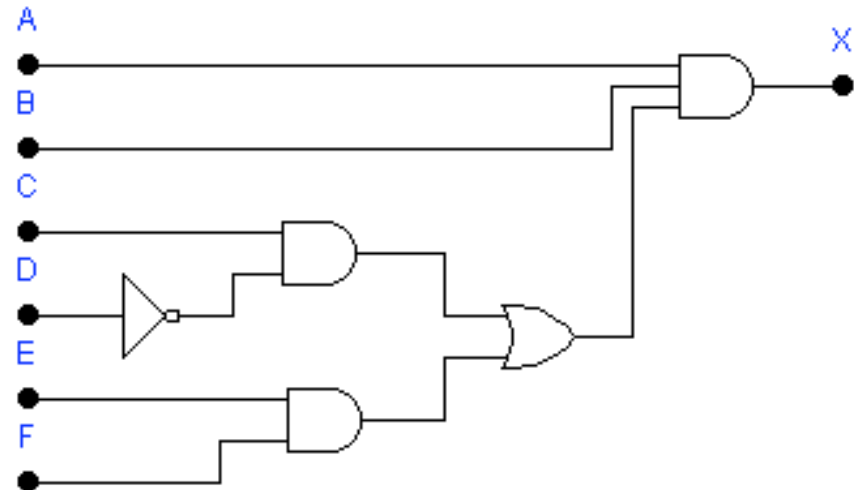Example 2

- Start with an expression
 $X = A.B. (C.D' + E.F)$



Putting it together



- From these simple components more complex circuits can be built to carry out essential functions. Eg.
 - comparison - comparator
 - arithmetic - adder, ALU
 - code conversion
 - encoding - encoder
 - decoding - decoder
 - data selection - multiplexer, demultiplexer
 - storage - flip-flops, registers
 - counting - counter
- Small and medium sized integration - circuits of < 100 gates


Boolean Algebra



- How to play around with the algebraic representation of a circuit.
- Why? - because it can lead us to better designs
 - efficient
 - cheaper
 - smaller

Example

■ $F = B \cdot ((A+B') \cdot (B+C))$

 

■ Needs 2 AND gates, 2 OR gates, 1 NOT gate, therefore is expensive.

■ **But** F is also $A \cdot B$

A	B	C	$A+B'$	$B+C$	$(A+B') \cdot (B+C)$	F	$A \cdot B$
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

■ We can show this using Boolean algebra (later)

Laws for OR

■ Basic laws for manipulating expressions using OR (+)


OR1 $A + 1 = 1$

OR2 $A + 0 = A$

OR3 $A + A = A$

OR4 $A + A' = 1$

■ Illustration of 1 and 2

 

Laws for AND

■ Basic laws for manipulating expressions using AND (.)


AND1 $A.1 = A$

AND2 $A.0 = 0$

AND3 $A.A = A$

AND4 $A.A' = 0$

■ Illustration of 1 and 2

 

Laws for NOT





- Basic law for manipulating expressions using NOT (')
NOT $(A')' = A$

Commutative laws

- It doesn't matter which order the inputs are in.

AND $A.B = B.A$

OR $A + B = B + A$

 
 


Associative laws

- It doesn't matter where the brackets are.

AND $(A.B).C = A.(B.C)$

OR $(A + B) + C = A + (B + C)$

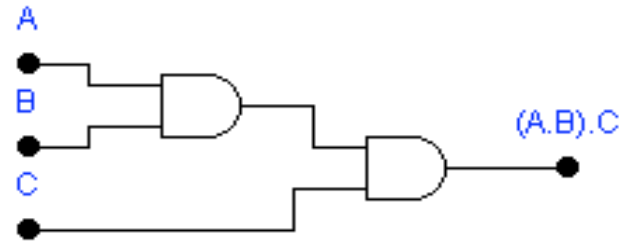 

- So, often we leave out the brackets.
- Note: this only works if they're all the same operator!
 - e.g. $(A.B) + C \neq A.(B + C)$



Distributive laws

■ Changing the top level operator.

DIST1 $(A.B) + C = (A + C).(B + C)$

DIST2 $(A + B).C = (A.C) + (B.C)$

DIST3 $A.(B + C) = A.B + A.C$

  

De Morgan's Laws

- **Very important!!**

- How to distribute a NOT inside a bracket.

DM 1 $(A + B)' = A'.B'$

DM 2 $(A.B)' = A' + B'$

- Why care about De Morgan's laws?

- Because we can turn an AND into an OR and vice versa.

- So if we only want one kind of gate (particularly NAND or NOR gates) in a circuit then De Morgan's laws help us derive that circuit.

Absorption Theorems

ABS1 $A + (A.B) = A$

ABS2 $A.(A + B) = A$

■ Proof of ABS1
... goes here ...

■ You can also verify by truth table

A	B	A + B	A.(A + B)
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1

■ Proof of ABS2
... goes here ...

More absorption



- $A + (A'.B) = A + B$

... proof goes here ...


- $A.(A' + B) = A.B$

... proof goes here ...

Applying Boolean Algebra: Example


- Show $(X + Y).(X' + Y') = ((X + Y)' + (X' + Y'))'$
- To give a NOR gate implementation

 Let $Z = (X + Y).(X' + Y')$
then $(Z')' = (((X + Y).(X' + Y'))')'$ NOT
 $= ((X + Y)' + (X' + Y'))'$ DM2



Going even further!

- We can even remove the NOT gates.

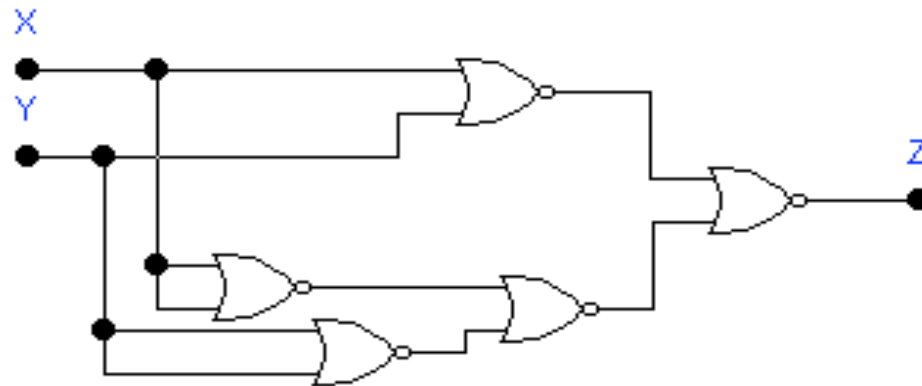


- making use of the equivalence $A' = (A + A)'$

Example (cont.)

- An alternative derivation:

$Z = \dots$

$$= X'.Y + X.Y'$$

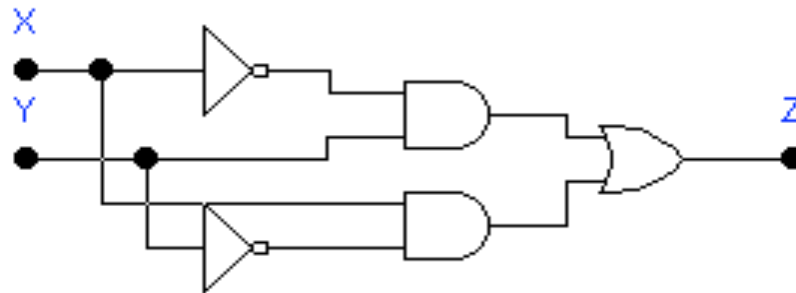


- Depends what kind of gates you want to use.

Complementation and De Morgan's laws

- Complement of A is A'; complement of A' is A (where A is any Boolean expression).
- Transformation using De Morgan's laws to obtain the complement of any expression.
- Substitute AND for OR and vice versa, and complement every literal.
- E.g.
$$(A.B)' = A' + B'$$
$$(A + B)' = A'.B'$$
- We'll come back to Boolean algebra again.

Combinational Logic Systems

 - **Definition:** A Combination Logic System (CLS) is a binary digital 'black box' system with a set of *inputs* and a set of *outputs*. Its *outputs* depend only on its current inputs (and not on the history of the system - there is no feedback)



- A major part of digital electronic design is the construction of more complex CLSs using the fundamental gates as building blocks.


Description of a CLS



- The operation of a CLS is completely described by its input/output relationship. This describes the value of the output for each and every possible combination of the inputs to the system.
- Two ways to do this:
 - Truth table
 - Boolean algebra

Truth Table for a CLS

 - Consider a CLS with N inputs and M outputs. There are 2^N possible combinations of inputs and therefore 2^N rows in the truth table. For each row M columns are required (one for each of the M outputs).
- **Example** 3 inputs (A, B, C), 2 outputs (X, Y).



- 2^3 rows = 8 rows
- 3 columns for inputs, 2 columns for outputs in each row.

Example (cont.)


A	B	C	X	Y
0	0	0	1	1
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	0

X and Y outputs depend on the particular CLS being described. A value for each of X and Y is required for every possible combination of inputs.

- Consider more inputs - Tedious!!
- A more compact description of the CLS is obtained using Boolean algebra (fewer gates = lower cost).

Boolean Functional Representation of a CLS

 - The operation of the CLS is given by the Boolean expression relating each output of the system to its inputs.
- **Example** (I/O as before)



- Let output X be $F_x = (A'.B')+(A'.C')+A.B.C$
- Let output Y be $F_y = (A.B.C)'$
- How do we move between the two representations?

Truth Table to Boolean Function

- Consider an N input, single output system.

- **Step 1:**

- Identify the rows in the truth table that give 1 at the output.

- **Step 2:**

- For each such row, write an expression containing all literals. Eg.

A	B	C	X	
⋮				
0	0	1	1	$A'.B'.C$
⋮				

- **Step 3:**

- Combine each such expression with the others using '+'.
This is a Boolean representation of the CLS.

Example


A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

■ $F_x = \text{????}$


- This form of Boolean expression has a special name: **The canonical sum of products form (CSOP)**
- Because it is the 'OR' of a set of 'AND' terms, and each 'AND' term contains all of the input literals or their complements.
- Each 'AND' term is called a *minterm*

Implementation of CSOP

 - The CSOP form suggests that the CLS is realised by a circuit consisting of a collection of 'AND' gates followed by a multi-input 'OR' gate. Each 'AND' gate implements a minterm, and the 'OR' gate gives the final output.
- E.g.



Example

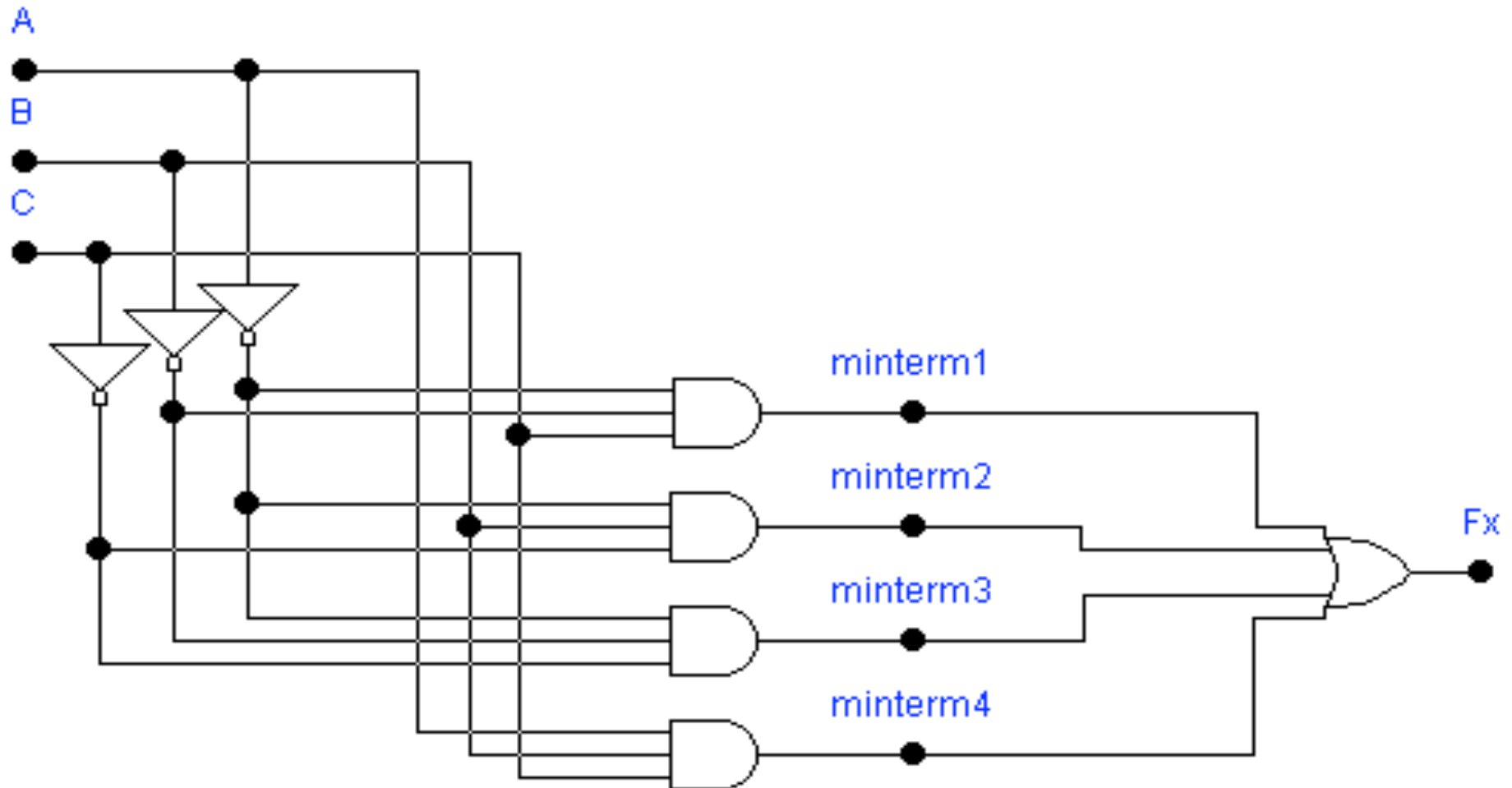

Conversion to NAND only

- The CSOP form may be written as

$$F_x = M_1 + M_2 + M_3 + \dots \quad \text{where } M_i \text{ are the minterms.}$$

- Therefore


$$\begin{aligned}(F_x)' &= (M_1 + M_2 + M_3 + \dots)' \\ &= M_1' \cdot M_2' \cdot M_3' \cdot \dots \quad \text{DM1}\end{aligned}$$

$$\begin{aligned}((F_x)')' &= (M_1' \cdot M_2' \cdot M_3' \cdot \dots)' \\ F_x &= (M_1' \cdot M_2' \cdot M_3' \cdot \dots)' \quad \text{NOT}\end{aligned}$$

- i.e. NAND representation (instead of using the OR gate of the previous implementation)
- Not only that, but each minterm is also implemented by a NAND gate

 Example

- E.g. let minterm $M_1 = A'.B'.C$
- Then we have



Design of a CLS



- So design of a CLS has 5 steps:
 1. Statement of the problem
 2. Assign I/O variables to letter symbols
 3. Derive a truth table defining the relationship between inputs and outputs
 4. Derive the Boolean functions for each output
 5. Draw the circuit diagram

Example: Half Adder

- Basic function - add two bits together: (weird name because in full adder you also consider the carry - so add 3 bits together)
- Variables
 - Input: A, B
 - Output: S(sum), C(carry)
- Truth Table

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


Half Adder (2)

- Boolean functions for S and C (in CSOP)

$$S = A'.B + A.B'$$

$$C = A.B$$

- Desired circuit is

 

Half Adder (3)


- Could also convert to NAND form

$$S' = (A'.B + A.B')' \quad C = ((A.B)')$$

$$= (A'.B)'.(A.B')'$$

$$S = (S')' = ((A'.B)'.(A.B')')'$$

 - To implement complement using NAND, note $A' = (A.A)'$



Half Adder and Full Adder

- These components are available as macros in DW.

- Schematic is



- Called a half adder because doesn't perform full adding function, but ok for LSB - no carry-in.

- Full Adder

- Required for other than LSB



Boolean expression to truth table

- Given a function F_x , first expand to CSOP form

$$F_x = (A+B).C'$$

$$= A.C' + B.C'$$

DISTR

$$= (A.C'.1) + (B.C'.1)$$

AND1

$$= (A.C'.(B + B')) + (B.C'.(A + A'))$$

OR4

$$= A.B.C' + A.B'.C' + A.B.C' + A'.B.C'$$

DISTR

$$= A.B.C' + A.B'.C' + A'.B.C'$$

OR3

- Then mark a 1 in the appropriate row.

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0